Electric Play Dough

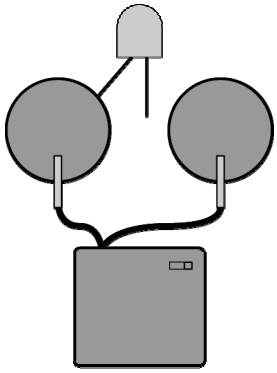
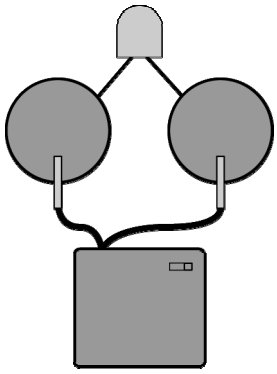
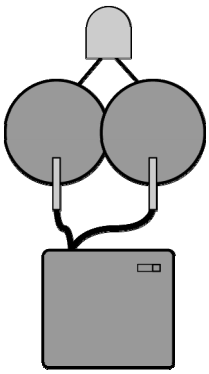
Name: _____

Student worksheet

Date: _____

Directions: Use this worksheet to record your observations.

1. Record what happens when you build a circuit using only conductive dough.

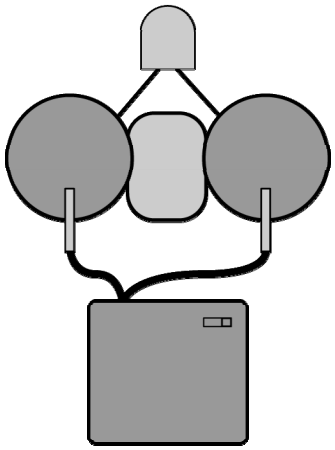
Type of Circuit	Picture	Observation
Open Circuit		
Closed Circuit		
Short Circuit		

Electric Play Dough—Page 2

Name: _____

Directions: Use this worksheet to record your observations.

2. Record what happens when you build a circuit using conductive and insulating dough.

Picture	Observation
	

3. Write down any other observations about your circuit.